Let's Make ...

Featured (/featured/)

Write an Instructable (thin (decount/gopro) | Sign Up (/account/gopro)

Classes (/classes/) Contests (/contest/)

ontest/) Forums (/community/?categoryGroup=all&category=all)


AND AND TO (DESKY Makeumything? (http://www.autodesk.com)

Teachers (/teachers/)

advertisement




Diet post-TAVR
Healthgrades

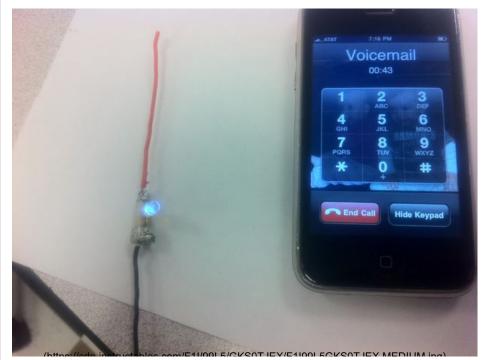







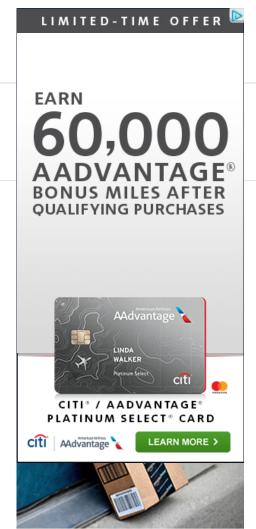

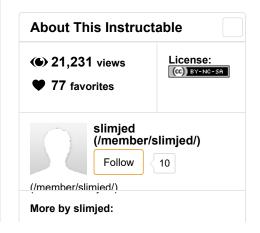This little-known trick can save you money on Amazon




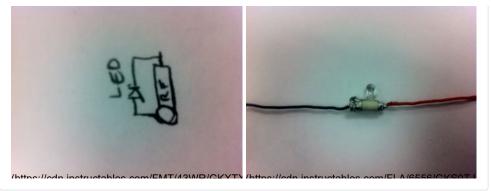


This simple circuit is able to detect signal from your cellphone antenna and converts it to electricity to power an LED (the best thing about this is that its completely passive and doesn't require batteries) this circuit requires: RF diode (search ebay for: RF diode or microwave diode) LED Peace of wire Solder I have Noticed that it only detects phones working on (EDGE), ocasionally works on 3G I have a low knowledge about RF but I think it has to de with the shape and/or length of antennas. So if you can contribute to make it work better please do so. (this is based on a video i saw a long time ago on you tube) the video had no instructions. here is the link http://www.youtube.com/watch? v=CNJVhzOjWgU&playnext=1&list=PL8ACFDE47FA548451 (RF energy, LED, tesla, passive, electricity)

Step 1: LED+RF Diode



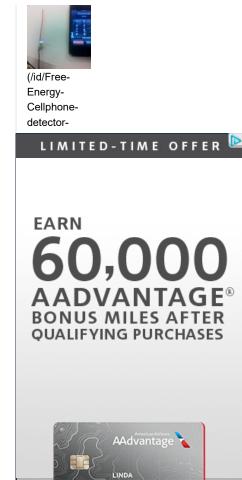




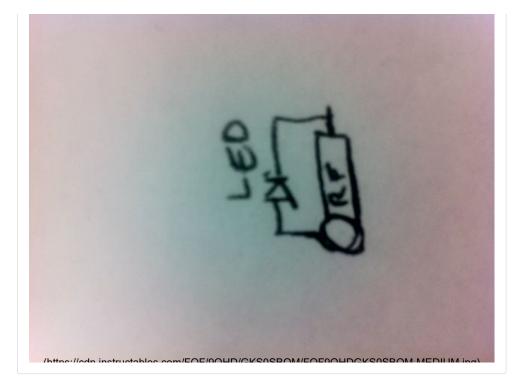

First Solder the led parallel to the Rf diode

Step 2: RF Diode+ LED+ Wires

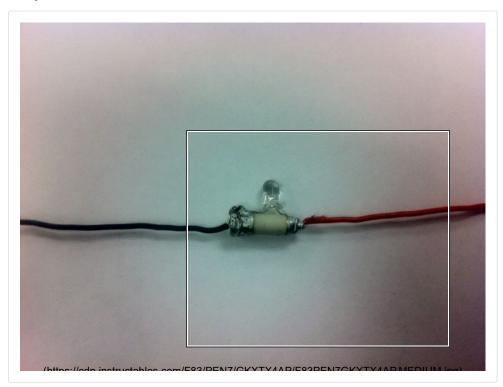

EARN
60,000
AADVANTAGE®
BONUS MILES AFTER
QUALIFYING PURCHASES

CITI® / AADVANTAGE®
PLATINUM SELECT® CARD

CITI® AAdvantage

LEARN MORE >

Solder One peace of wire to each end of the RF diode which will work as antenna

Step 3: Make a Call and Put the Circuit Next to Phone